 


LABORATORY 8

1. VHDL CODE FOR FULL ADDER DATA FLOW:



Full Adder				
A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



EXPRESSIONS:

$$S = A \oplus B \oplus Ci$$
$$CO = (A \oplus B)Ci + AB$$

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity fa1 is
    Port ( a,b,ci : in STD_LOGIC; s,co : out STD_LOGIC);
end fa1;

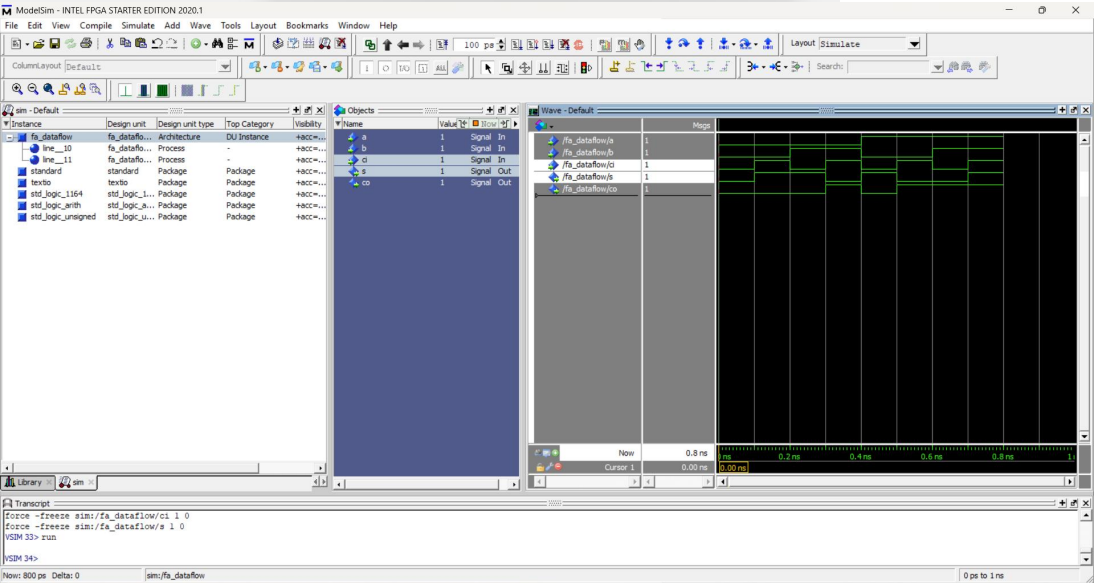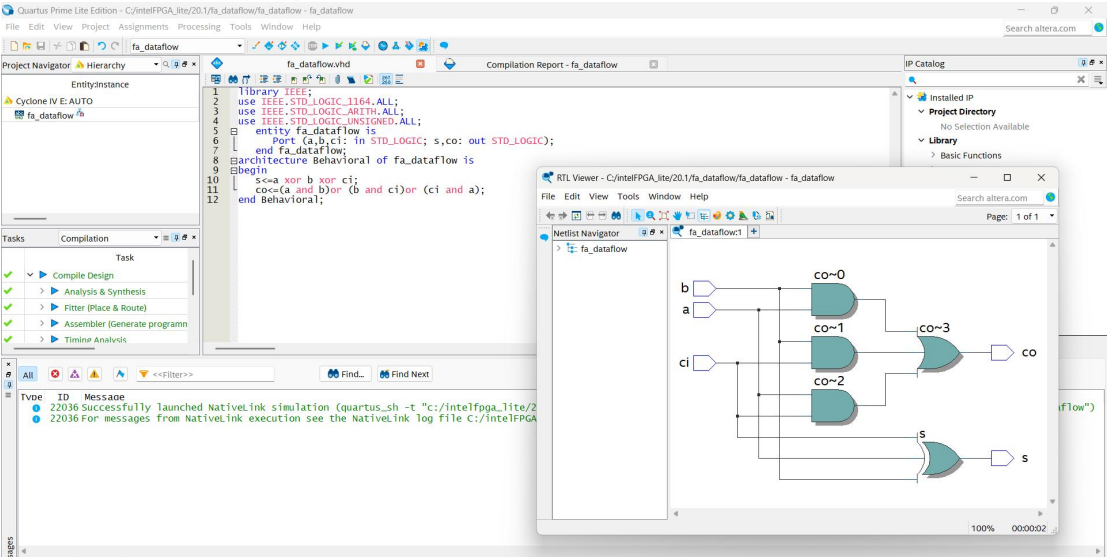architecture Behavioral of fa1 is
begin
    s<=a xor b xor ci;
    co<=(a and b)or (b and ci)or (ci and a);
end Behavioral;
```



VHDL CODE FOR FULL ADDER BEHAVIORAL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity fa1 is
    Port ( a,b,ci : in STD_LOGIC; s,co : out STD_LOGIC);
end fa1;
architecture Behavioral of fa1 is
begin
    process(a,b,ci)
    begin
        s<=a xor b xor ci;
        co<=(a and b)or (b and ci)or (ci and a);
    end process;
end Behavioral;
```

